
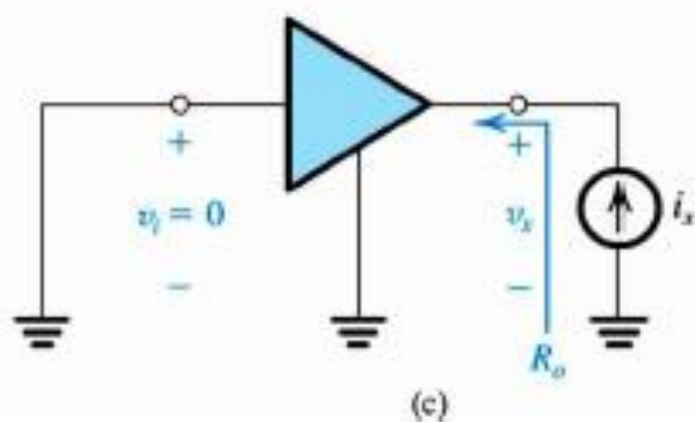
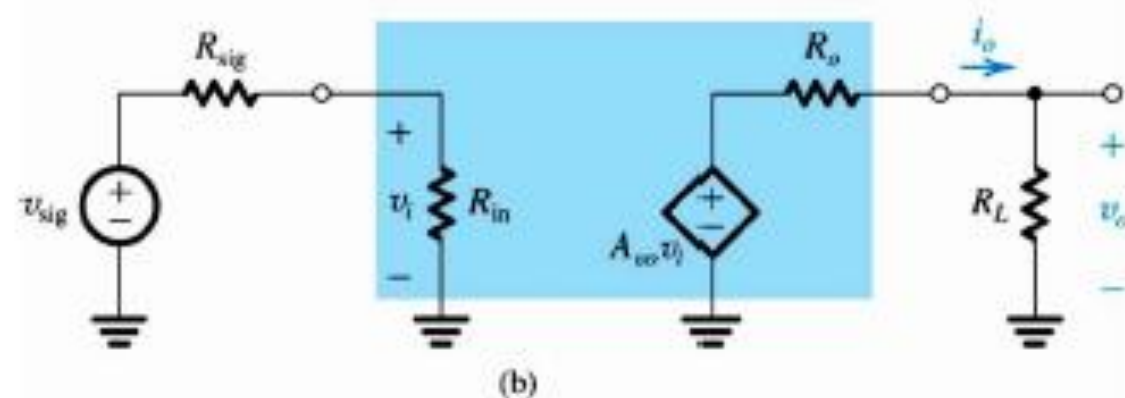


Lec-8

Characterizing Amplifiers

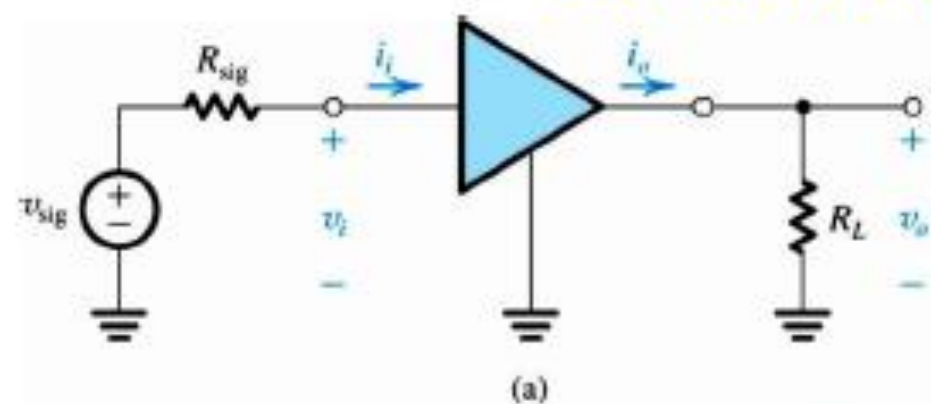

$$R_{in} \equiv \frac{v_i}{i_i} \quad v_i = \frac{R_{in}}{R_{in} + R_{sig}} v_{sig}$$

$$A_{vo} \equiv \left. \frac{v_o}{v_i} \right|_{R_L = \infty} \quad R_o = \frac{v_x}{i_x}$$

$$v_o = \frac{R_L}{R_L + R_o} A_{vo} v_i$$


$$A_v \equiv \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_o}$$

$$G_v \equiv \frac{v_o}{v_{sig}} \quad G_v = \frac{R_{in}}{R_{in} + R_{sig}} A_v$$

The Common-Emitter (CE) Amplifier


$$r_{\pi} = \frac{\beta}{g_m} \quad g_m = \frac{I_C}{V_T}$$

$$r_o = |V_A| / I_C$$

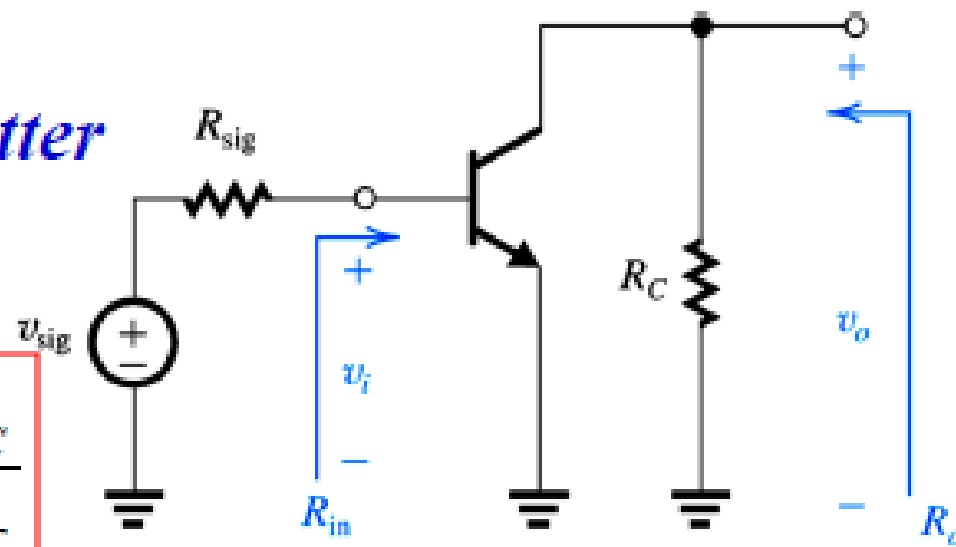


(a)
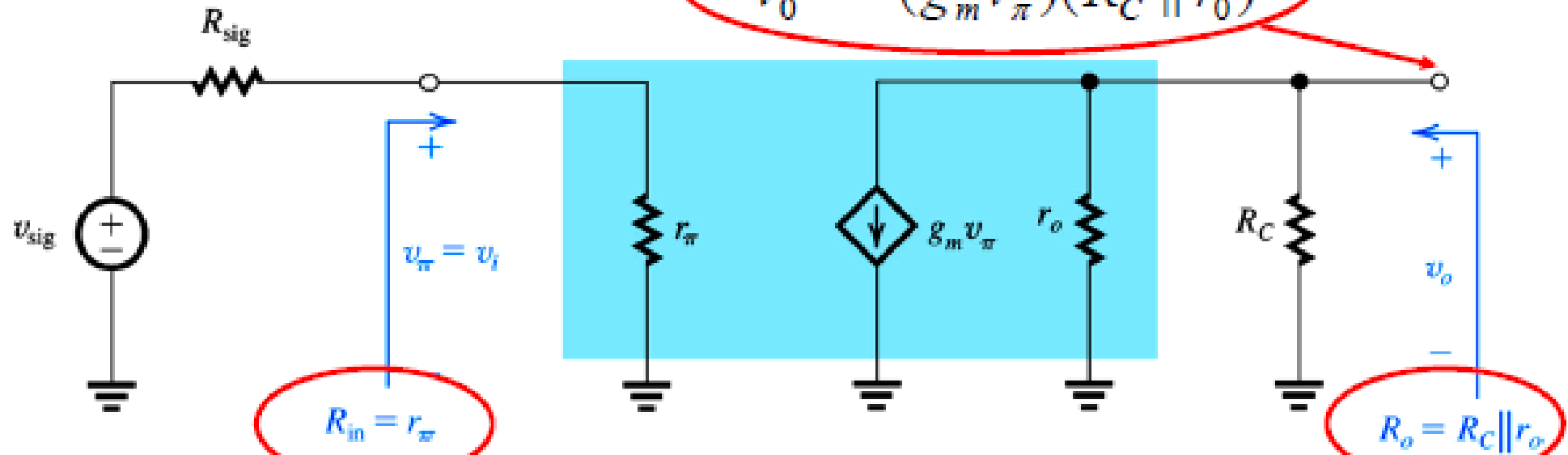
$$v_o = -(g_m v_{\pi})(R_C \parallel r_o)$$



(b)

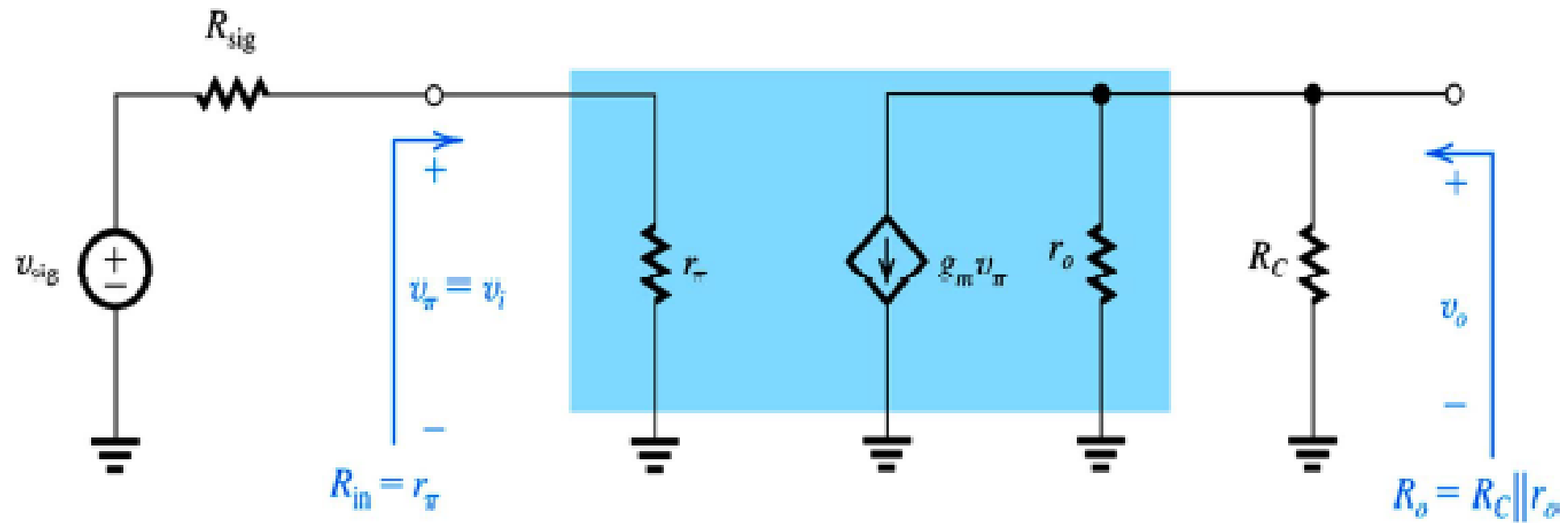

(b)


$$v_i = v_{\pi} \quad A_{v0} \equiv \frac{v_o}{v_i}$$

$$A_{v0} = -g_m (R_C \parallel r_o)$$

$$R_o \approx R_C \quad (r_o \text{ is large})$$

$$A_v = -g_m (R_C \parallel R_L \parallel r_o)$$
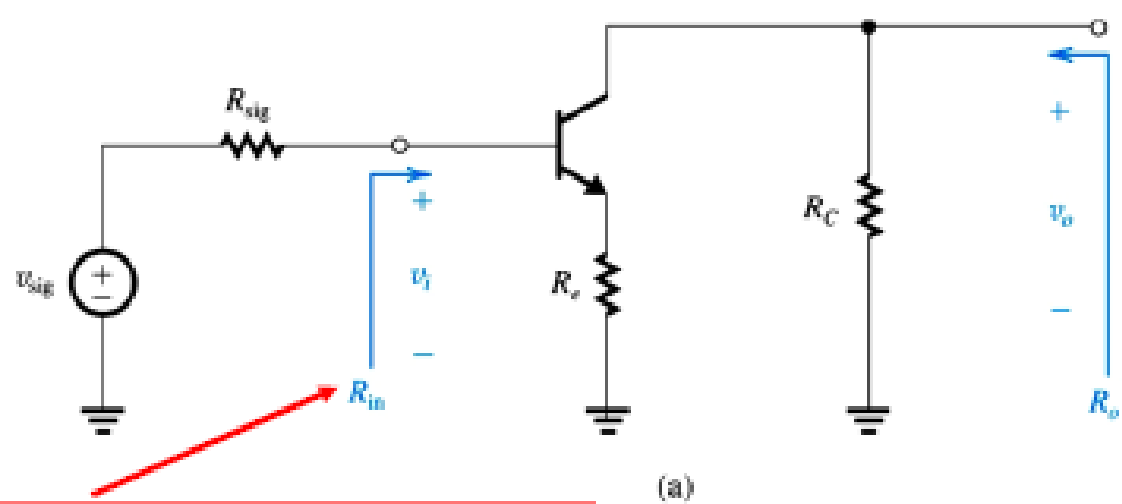
$$G_v \equiv \frac{v_o}{v_{sig}} = -\frac{r_{\pi}}{r_{\pi} + R_{sig}} g_m (R_C \parallel R_L \parallel r_o)$$




CE amplifier with an emitter resistance R_e

$$R_o = R_C$$

$$R_{in} = (\beta + 1)(r_e + R_e)$$


important

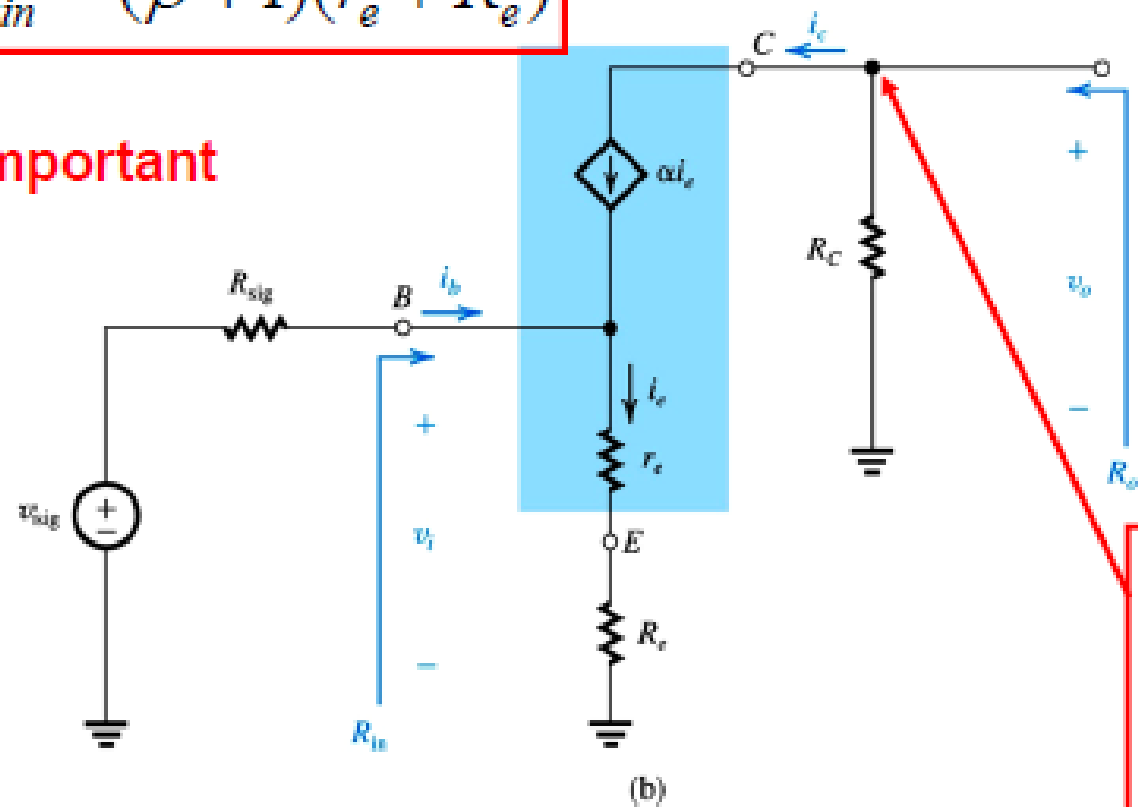


$$A_{vo} = -\frac{g_m R_C}{1 + \frac{R_e}{r_e}} \cong -\frac{g_m R_C}{1 + g_m R_e}$$

Lec-9

CE-AMP. using Current Source Biasing

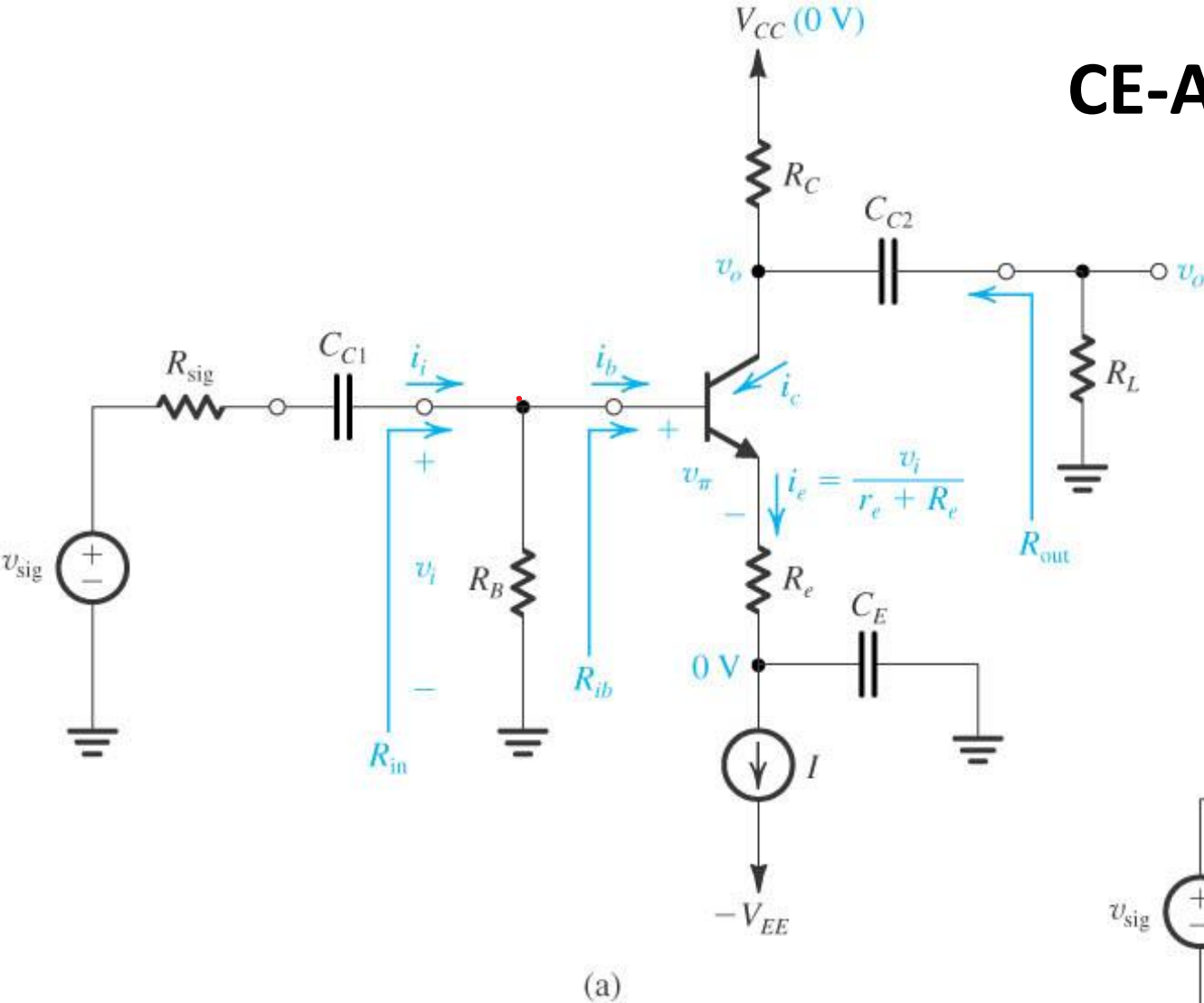

(a)

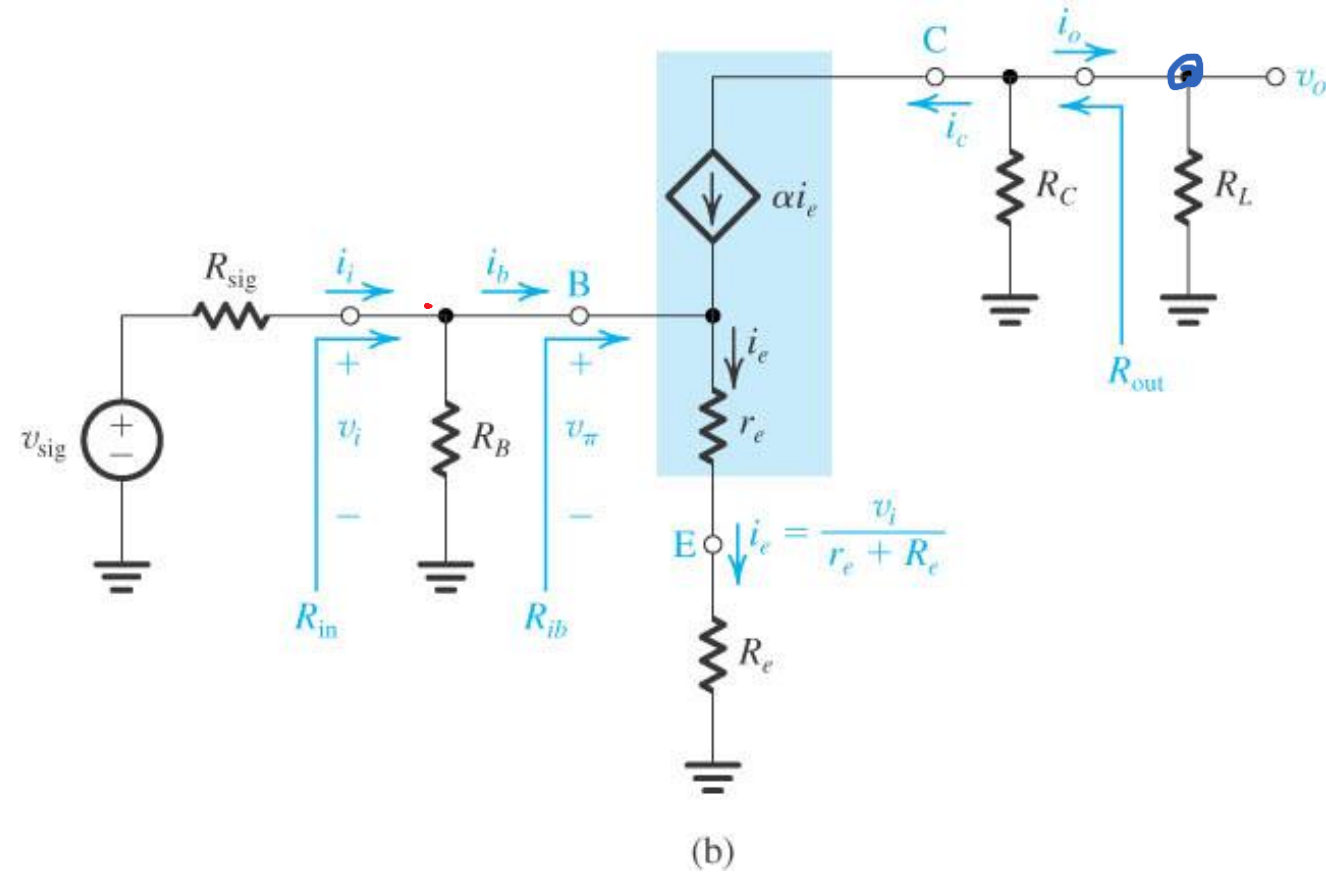

(b)

H.W. (self study)
Obtain R_{in} , R_{out} and A_{vo}

Review concepts to analyse any amplifier configuration

- External Capacitors (μF) are used to couple AC input signal/ DC blocking/ Bypass capacitor.
- For DC- these are assumed to be open ckt for DC analysis.
- To be considered as short ckt for AC analysis i.e. Small Signal Analysis for Mid frequency band (kHz).
- Internal Device capacitors (pF) also assumed open ckt.


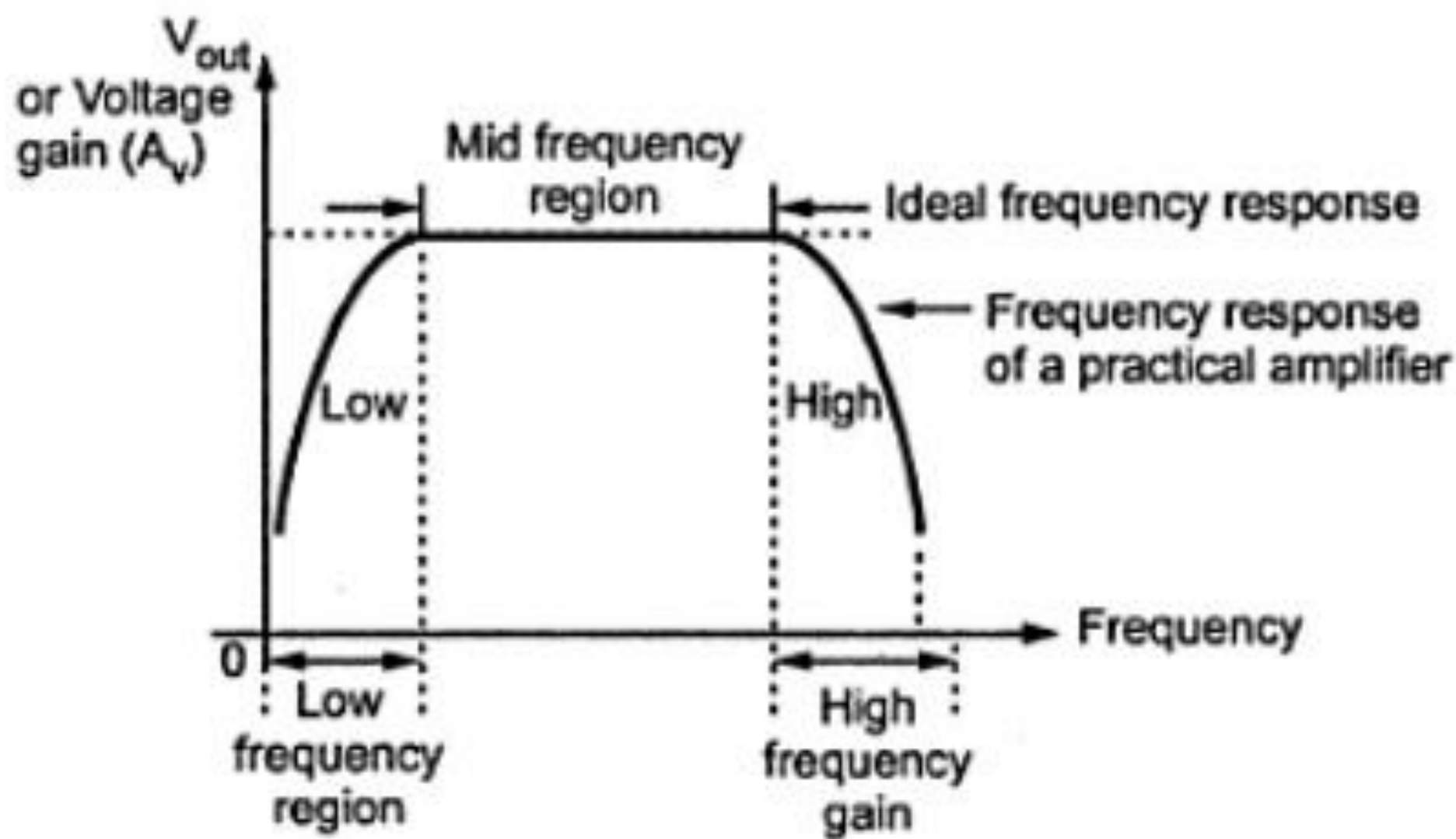
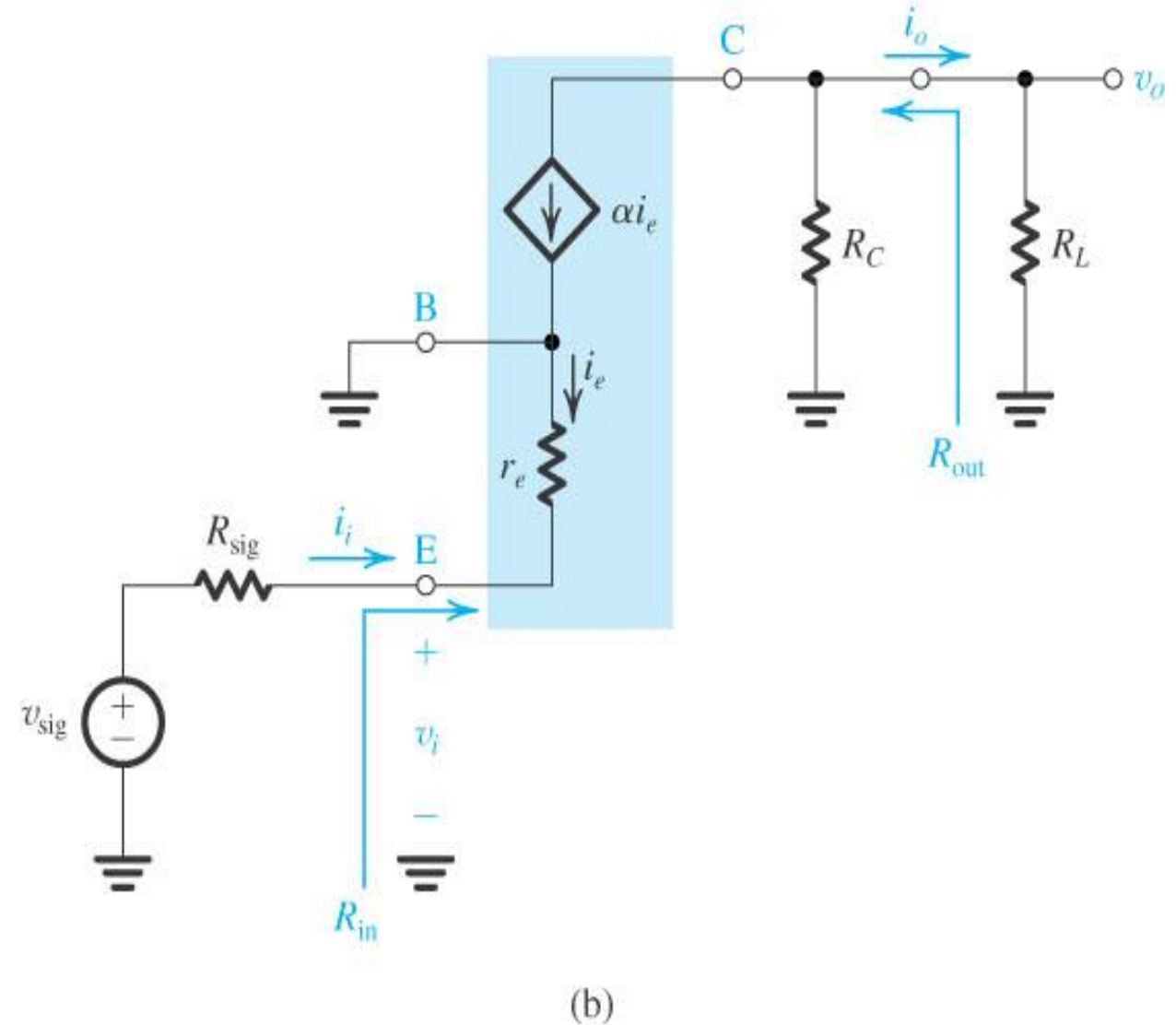


Fig. A typical frequency response of an amplifier


Common Base and Common Collector Amp. Small Signal -AC analysis

CB-Amplifier

(Small Signal AC analysis)

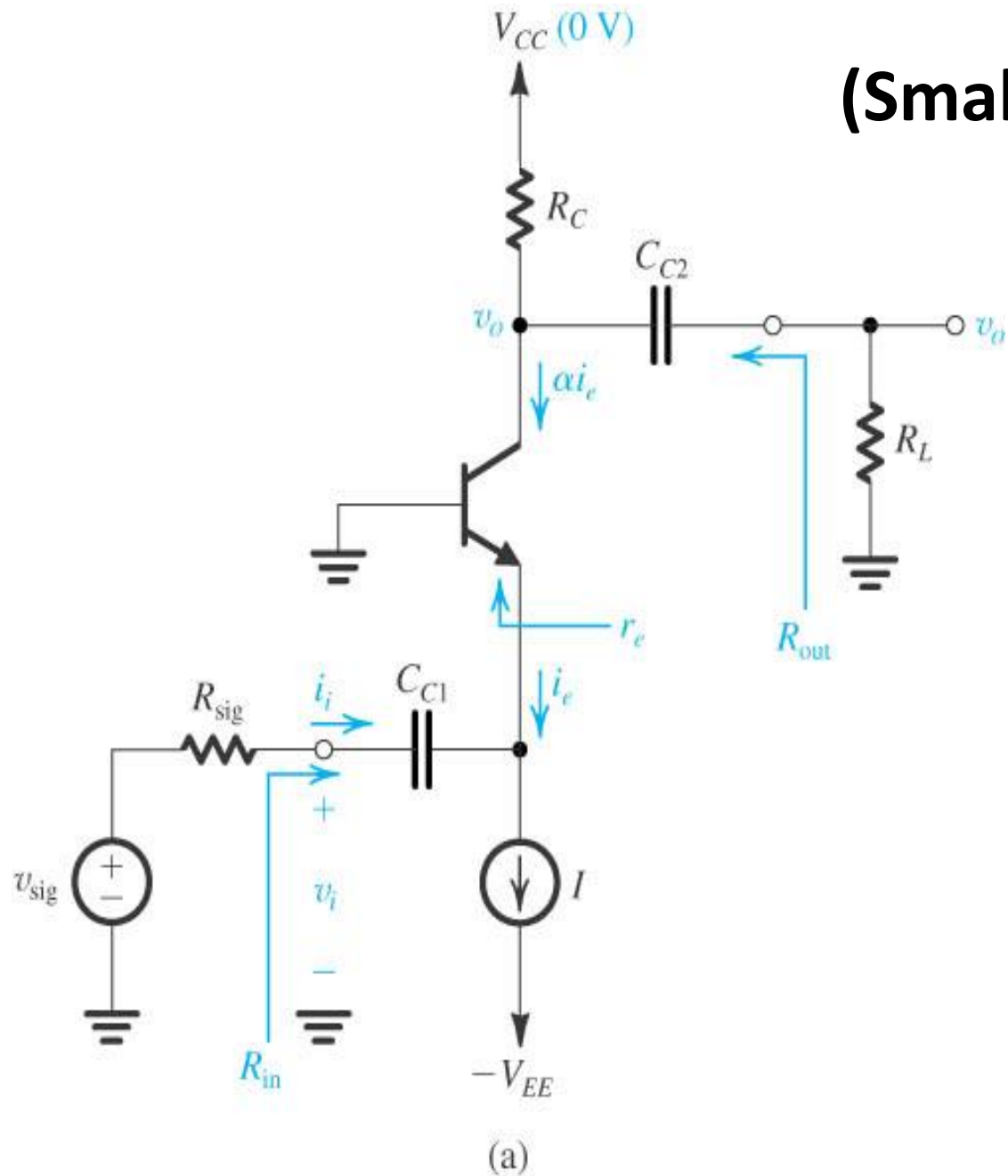


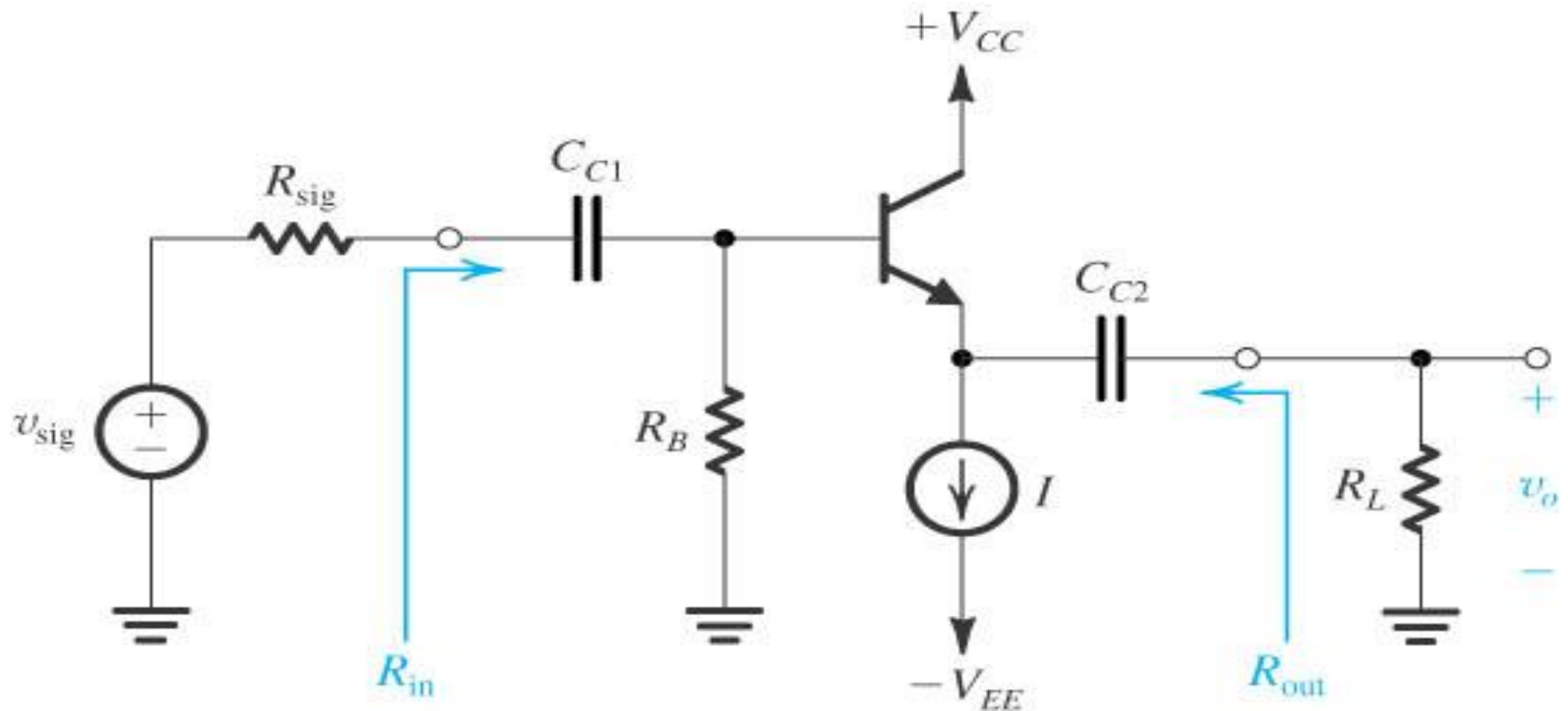CC-Amplifier/Emitter Follower/ Voltage Buffer




(a)


Small Signal Equivalent (CC config.)

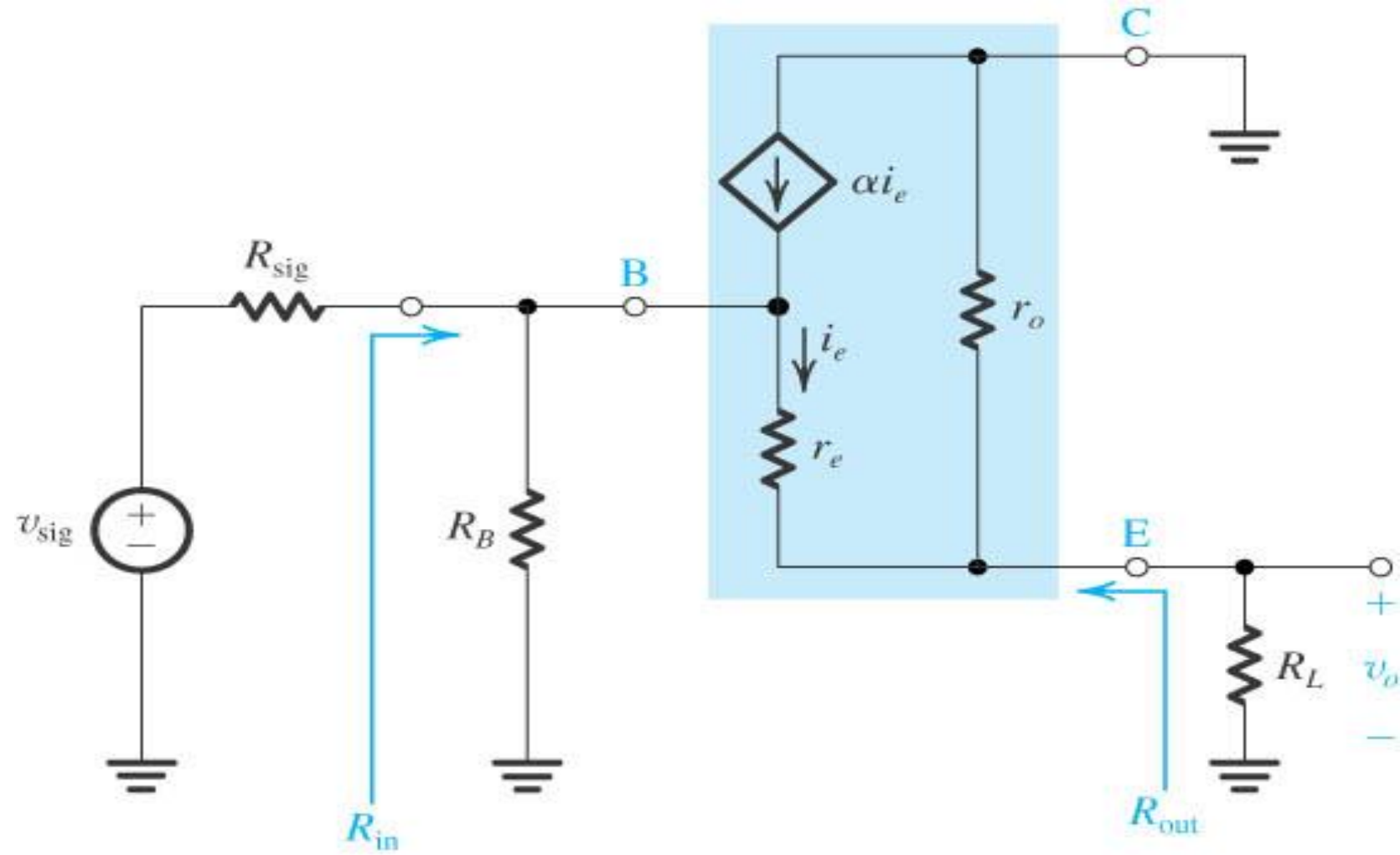

(b)

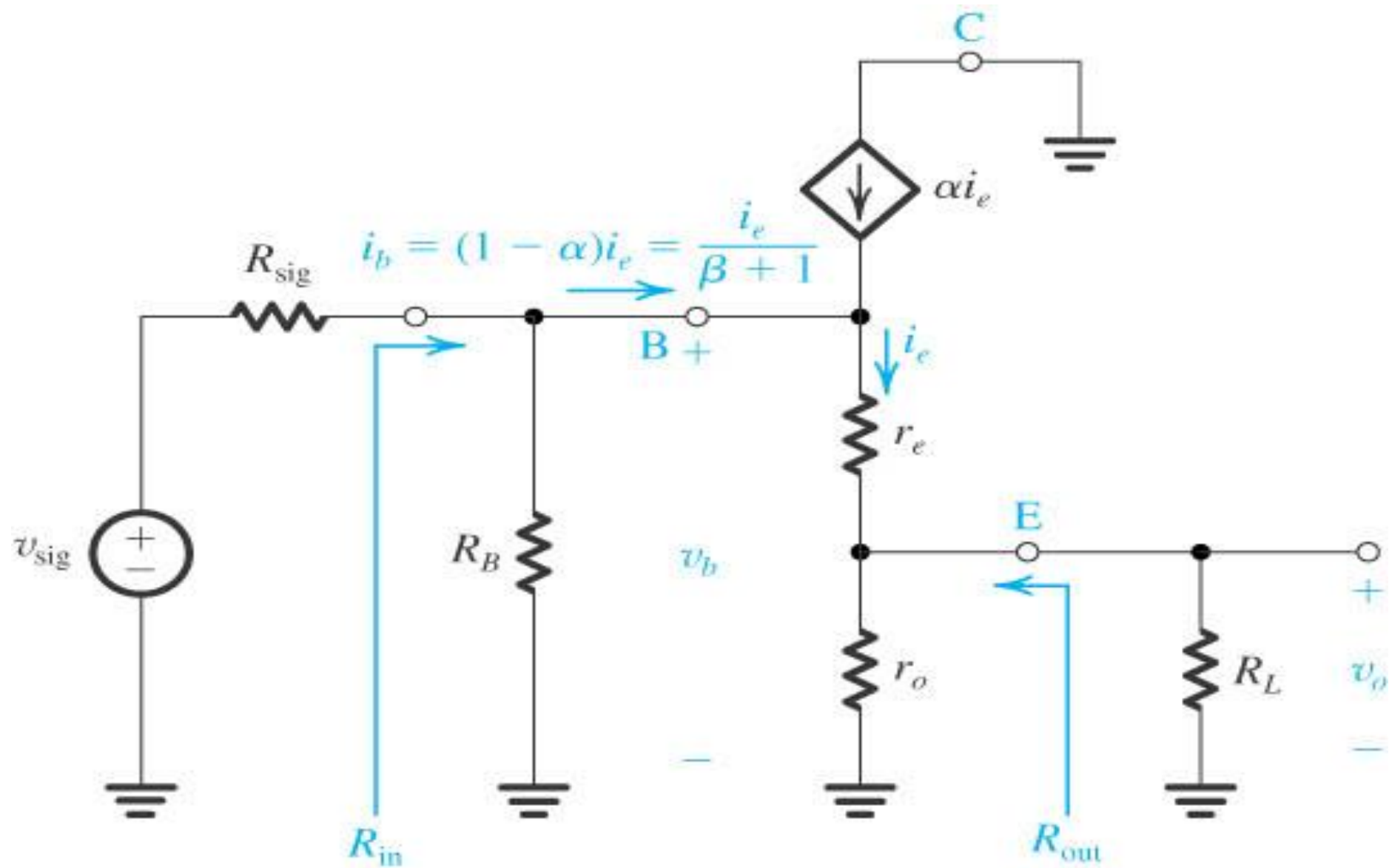


(c)

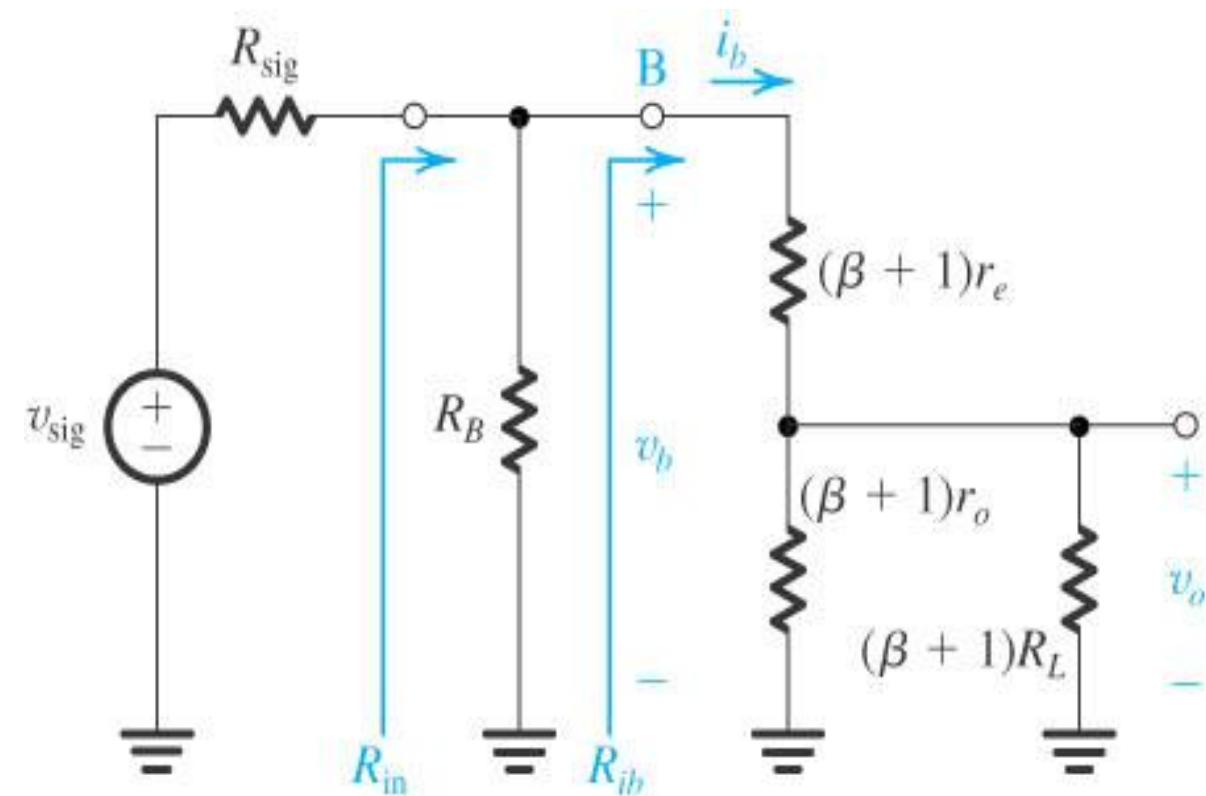


$$R_{in} = R_B // (\beta + 1)[r_e + (r_o // R_L)]$$

(a)

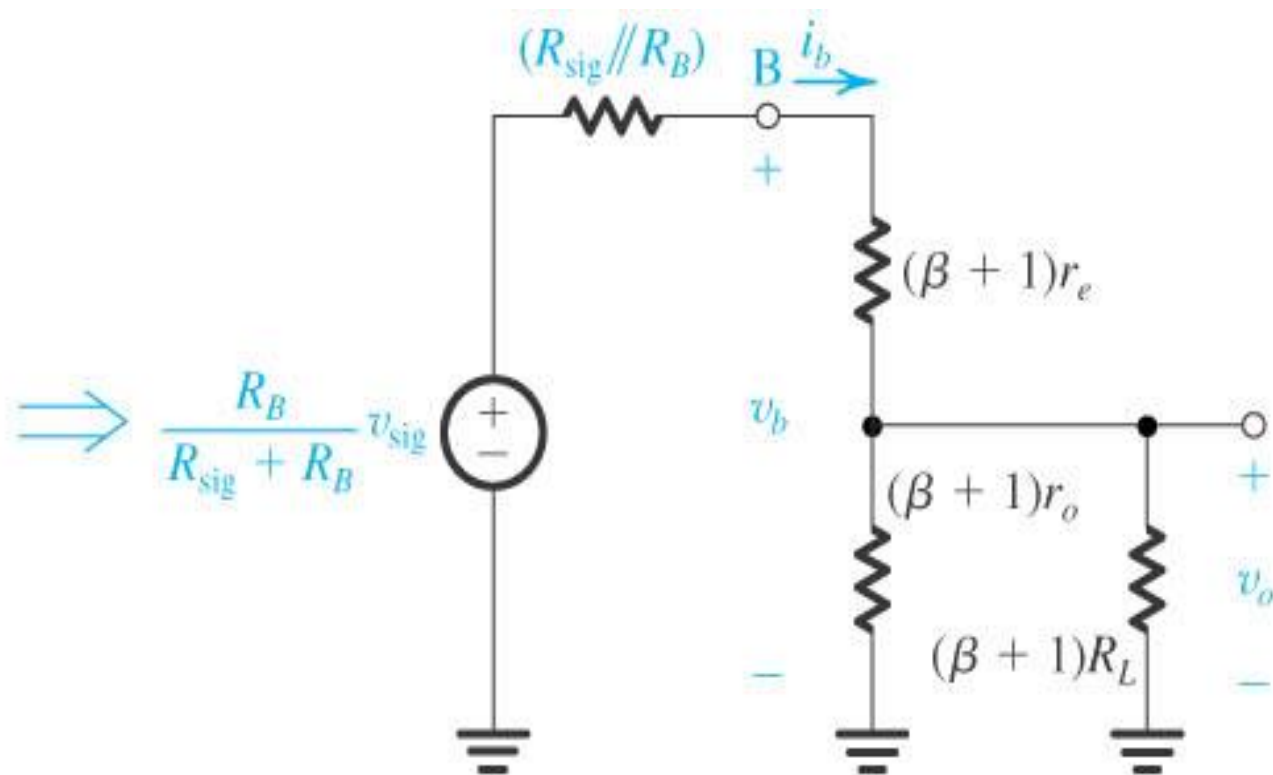


$$G_v = \frac{v_o}{v_{sig}} = \frac{R_B}{R_{sig} + R_B} \frac{(\beta + 1)(r_o // R_L)}{(R_{sig} // R_B) + (\beta + 1)[r_e + (r_o // R_L)]}$$

(b)

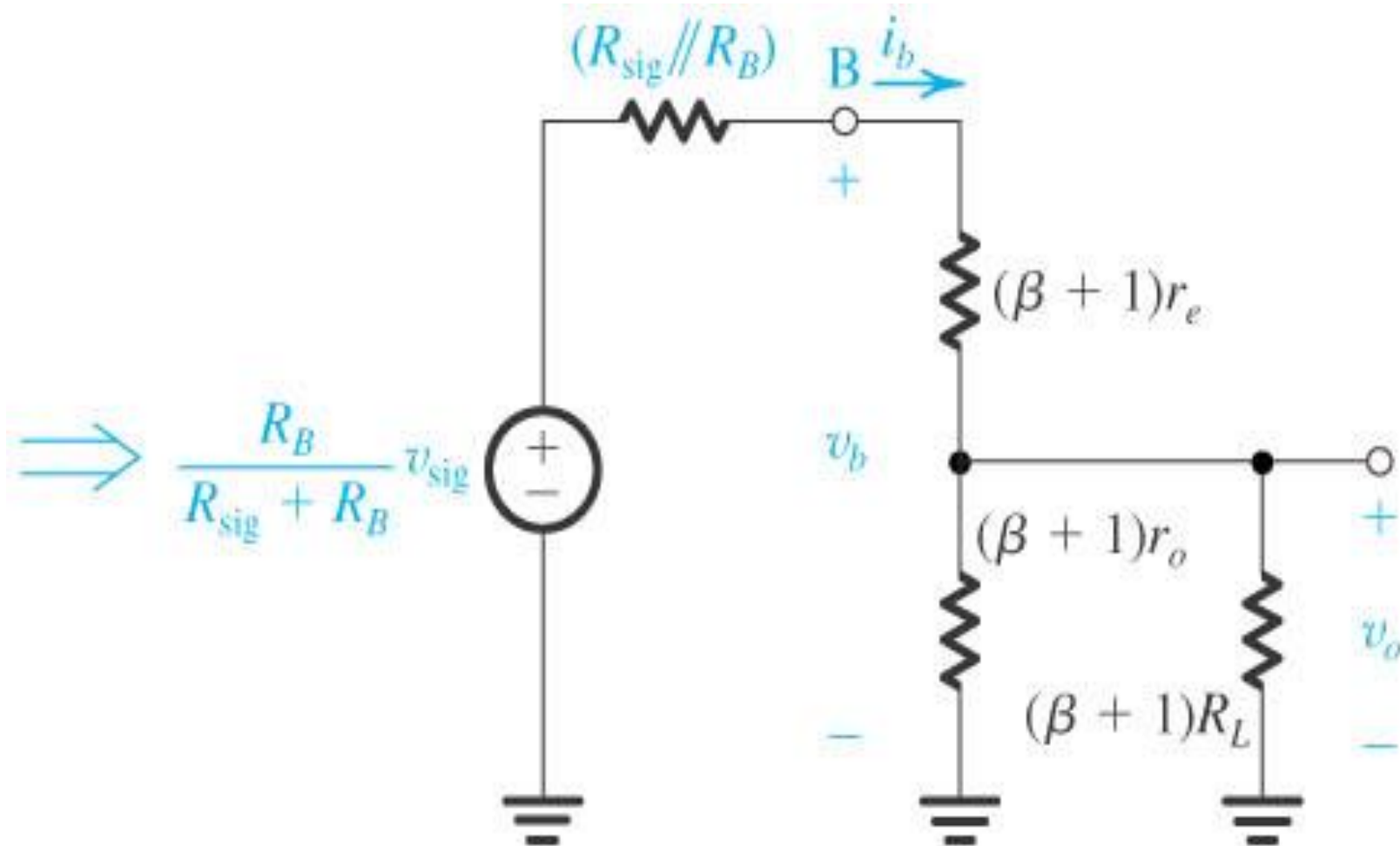

$$G_v = \frac{v_o}{v_{sig}} = \frac{R_B}{R_{sig} + R_B} \frac{(\beta + 1)(r_o \parallel R_L)}{(R_{sig} \parallel R_B) + (\beta + 1)[r_e + (r_o \parallel R_L)]}$$

(b)

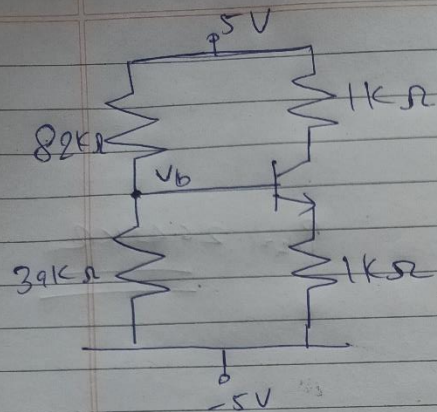


$$R_{th} = \frac{39 \times 82}{39 + 82}$$

$$R_{th} = 26.43 k\Omega$$

$$+5V - 82kI_a - 39kI_a - (-5V) = 0$$

$$I_a = \frac{10}{121k}$$


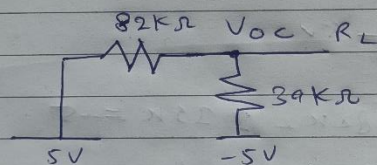


$$V_{oc} = 5 - 82kI_a$$

$$= 5 - 82 \times \frac{10}{121k}$$

$$V_{oc} = -1.78V$$

$$V_{oc} = V_{th} = -1.78V$$

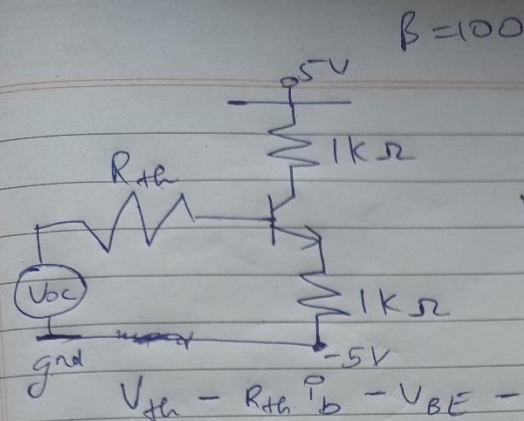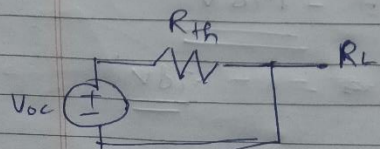

$$\beta = 100$$

$$I_c = I_e = \beta I_b$$

$$= 100 I_b$$

$$V_{oc} = V_{th} = -1.68V$$

$$R_{th} = 26.43k$$

$$I_c = I_e$$

$$V_{th} - R_{th} I_b - V_{BE} - 1k I_e = -5$$

$$-1.78 - 26.43k I_b - 0.7 - 5 = 26.43k I_b + 100 I_b$$

$$I_b = \frac{2.52V}{126.43k\Omega}$$

$$I_b = 20\mu A$$

$$I_c = I_e = 2mA$$

$$5 - 1k I_c - V_{CE} - 1k I_e + 5 = 0$$

$$V_{CE} = 10 - 2k \times 2mA$$

$$= 6V$$

$$V_{CE} = 6V$$

$$I_c = I_e = 2mA \quad I_b = 20\mu A$$

Thanks